

05/11/2025

# Revisão - Aula - Shrogo grata

## Eng Elétrica 10N

$$\begin{aligned} 1- V_{an} &= 100 \angle 0^\circ V & R_a &= 10 \Omega & a &= 1 \angle 120^\circ \\ V_{bn} &= 50 \angle -120^\circ V & R_b &= 40 \Omega & a^2 &= 1 \angle 240^\circ \text{ ou } 1 \angle -120^\circ \\ V_{cn} &= 80 \angle 100^\circ V & R_c &= 10 \Omega \end{aligned}$$

$$\begin{aligned} I_a^0 &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \times \begin{bmatrix} 10 \angle 0^\circ \\ 1,25 \angle -120^\circ \\ 8 \angle 100^\circ \end{bmatrix} = \begin{bmatrix} 100 \angle 0^\circ V \\ 50 \angle -120^\circ V \\ 80 \angle 100^\circ V \end{bmatrix} \\ I_a^1 &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \times \begin{bmatrix} 10 \angle 0^\circ \\ 1,25 \angle -120^\circ \\ 8 \angle 100^\circ \end{bmatrix} \\ I_a^2 &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \times \begin{bmatrix} 10 \angle 0^\circ \\ 1,25 \angle -120^\circ \\ 8 \angle 100^\circ \end{bmatrix} \end{aligned}$$

$$\begin{aligned} I_a^0 &= \frac{1}{3} \begin{bmatrix} 10 \angle 0^\circ & 1,25 \angle -120^\circ & 8 \angle 100^\circ \end{bmatrix} = \begin{bmatrix} 3,49 \angle 40,40^\circ \\ 6,32 \angle -8,29^\circ \\ 1,73 \angle -51,35^\circ \end{bmatrix} \\ I_a^1 &= \frac{1}{3} \begin{bmatrix} 10 \angle 0^\circ & 1,25 \angle -120^\circ & 8 \angle 100^\circ \end{bmatrix} \\ I_a^2 &= \frac{1}{3} \begin{bmatrix} 10 \angle 0^\circ & 1,25 \angle -120^\circ & 8 \angle 100^\circ \end{bmatrix} \end{aligned}$$

$$\begin{aligned} I_a^0 &= 3,49 \angle 40,40^\circ \\ I_a^1 &= 6,32 \angle -8,29^\circ \\ I_a^2 &= 1,73 \angle -51,35^\circ \end{aligned}$$






$$\begin{aligned} V_a^0 &= \frac{1}{3} \begin{bmatrix} 100 \angle 0^\circ & 50 \angle -120^\circ & 80 \angle 100^\circ \end{bmatrix} = \begin{bmatrix} 23,55 \angle 39,14^\circ \\ 75,61 \angle -6,93^\circ \\ 5,31 \angle -30,63^\circ \end{bmatrix} \\ V_a^1 &= \frac{1}{3} \begin{bmatrix} 100 \angle 0^\circ & 50 \angle -120^\circ & 80 \angle 100^\circ \end{bmatrix} \\ V_a^2 &= \frac{1}{3} \begin{bmatrix} 100 \angle 0^\circ & 50 \angle -120^\circ & 80 \angle 100^\circ \end{bmatrix} \end{aligned}$$

$$S = P + jQ = 3 V_a^1 I_a^{1*} + 3 V_a^2 I_a^{2*} + 3 V_a^0 I_a^{0*}$$


$$\begin{aligned} S &= (3 \cdot 75,61 \angle -6,93^\circ \cdot 6,32 \angle 8,29^\circ + 3 \cdot 5,31 \angle -30,63^\circ \cdot 1,73 \angle 51,35^\circ) \\ &+ (3 \cdot 23,55 \angle 39,14^\circ \cdot 3,49 \angle -40,40^\circ) \end{aligned}$$
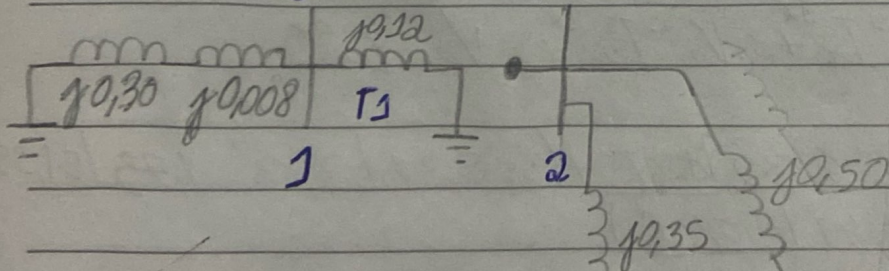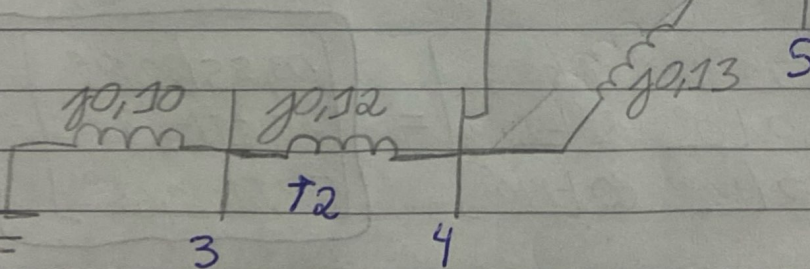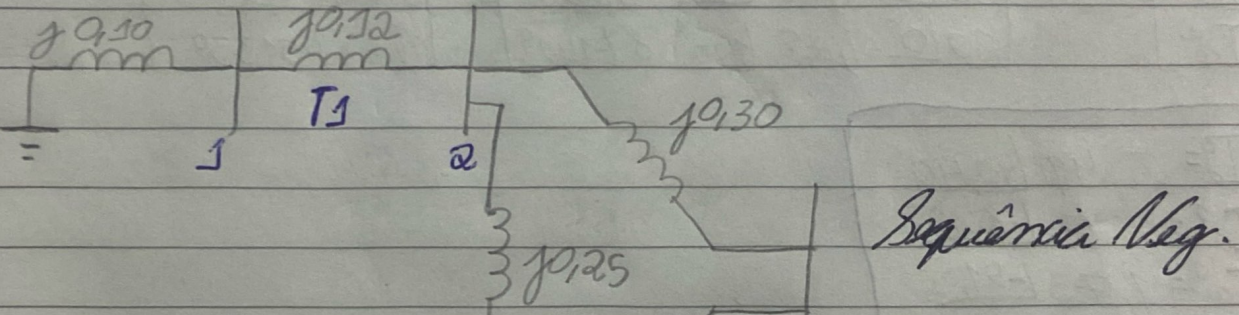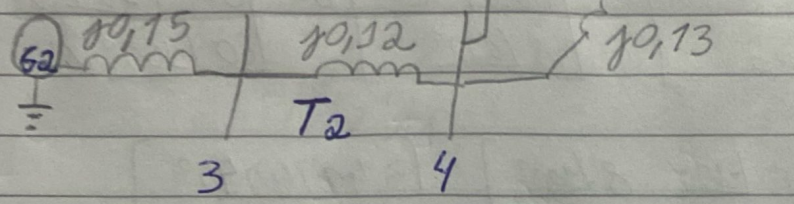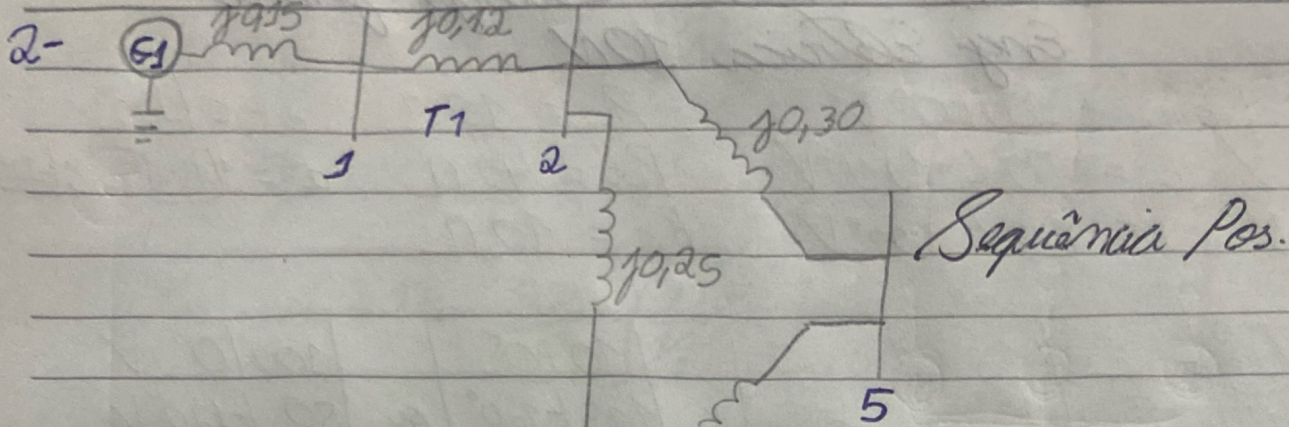
$$S = 1701 \text{ VA ou } 1,70 \text{ kVA}$$





*Sequência zero*

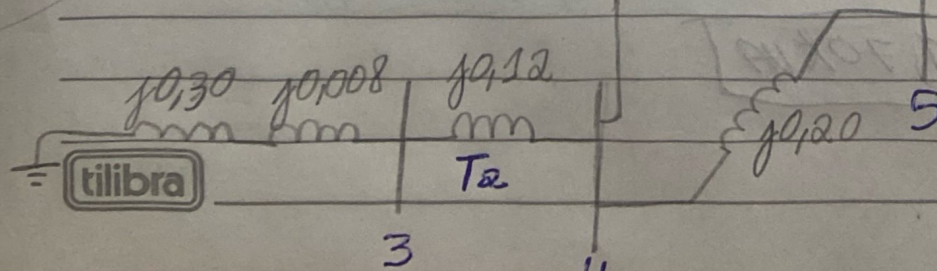



$$3- V_{bA} = 33 \text{ KV}$$

$$V_{bB} = \frac{110}{32} \cdot 33 \text{ KV} = 113,43 \text{ KV}$$

$$V_{bC} = V_{bB} = 113,43 \text{ KV}$$

$$V_{bD} = \frac{32}{110} \cdot 113,43 \text{ KV} = 33 \text{ KV}$$

$$Z_{T1}^{pu} = 0,08 \cdot \frac{100}{110} \cdot \left( \frac{110 \text{ KV}}{113,43 \text{ KV}} \right)^2 = 0,0683 \text{ pu}$$

$$Z_{T2}^{pu} = 0,08 \cdot \frac{100}{110} \cdot \left( \frac{32}{33} \right)^2 = 0,0683 \text{ pu}$$

$$Z_{LTbase} = \frac{(V_{bB})^2}{S_{base}} = \frac{(113,43)^2}{100} = 128,66 \Omega$$




$$Z_{LT}^{pu} = \frac{Z_{LT}}{Z_{LTbase}} = \frac{60}{128,66} = 0,466 \text{ pu}$$

$$Z_{m1}^{pu} = 0,2 \cdot \frac{100}{40} \cdot \left( \frac{30}{33} \right)^2 = 0,413 \text{ pu}$$

$$Z_{m2}^{pu} = 0,2 \cdot \frac{100}{30} \cdot \left( \frac{30}{33} \right)^2 = 0,551 \text{ pu}$$
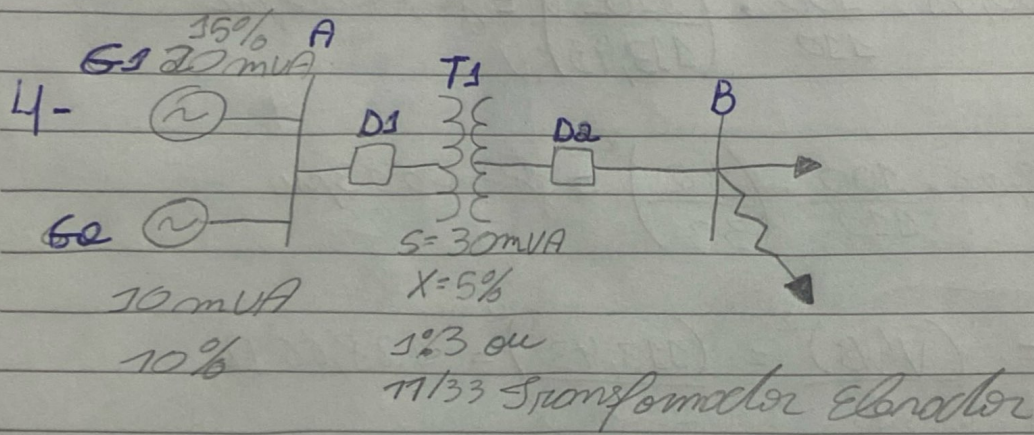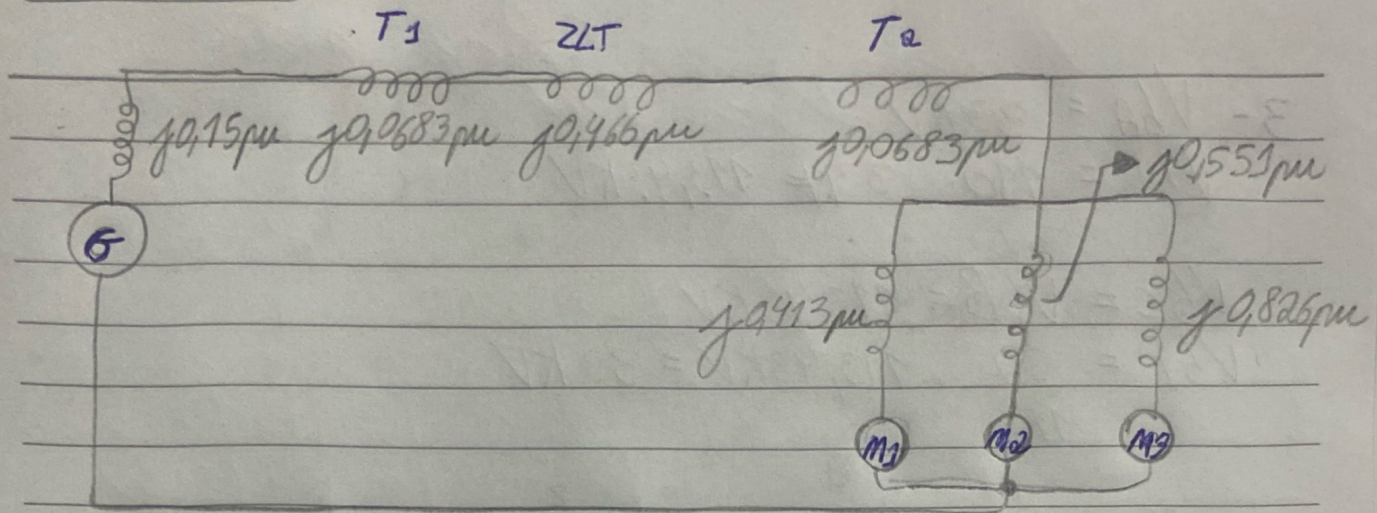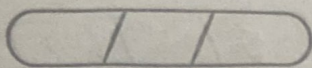
$$Z_{m3}^{pu} = 0,2 \cdot \frac{100}{20} \cdot \left( \frac{30}{33} \right)^2 = 0,826 \text{ pu}$$





$$X_{G1} = j0,15 \cdot \frac{30}{20} \cdot \left(\frac{11}{11}\right)^2 = j0,225 \text{ pu}$$


$$X_{G2} = j0,1 \cdot \frac{30}{10} \cdot \left(\frac{11}{11}\right)^2 = j0,3 \text{ pu}$$

$$X_{T1} = j0,05 \cdot \frac{30}{30} \cdot \left(\frac{11}{11}\right)^2 = j0,05 \text{ pu}$$

$$R_b = \frac{(V_b)^2}{S_b} = \frac{(33)^2}{30} = 36,3 \, \Omega$$
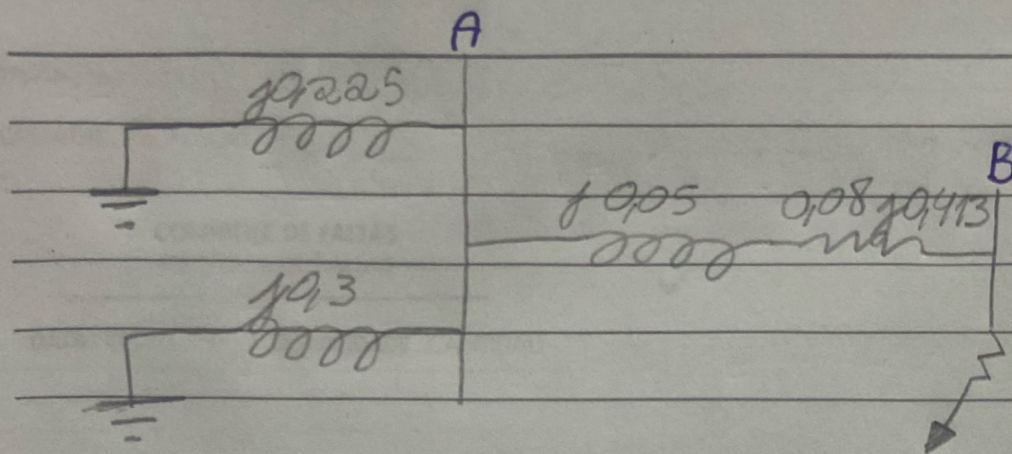
$$Z_{LT} = \frac{3 + j15}{36,30} = 0,08 + j0,413$$





$$Z_{th} = (j0.08 + j0.413 + j0.05) + (j0.225 \parallel j0.3)$$

$$Z_{th} = j0.08 + j0.463 + j0.128$$

$$Z_{th} = j0.596 \mu$$

$$I_{CC3}^{\mu} = \frac{I_{\mu}}{Z_{th}} = j1.676 \mu$$

$$I_b = \frac{S_b}{\sqrt{3} V_b} \quad S_b = \sqrt{3} V_b I_b$$

$$I_b = \frac{30 \cdot 10^6}{\sqrt{3} \cdot 33 \cdot 10^3} = 524.86 A$$

$$I_{CC3} = I_{CC3}^{\mu} \cdot I_b = j1.676 \times 524.86 = 879.96 A$$

$$S = \sqrt{3} V_L I_{CC}$$

$$S = \sqrt{3} \cdot 33 \cdot 10^3 \cdot 879.96 A = \boxed{50 mVA}$$